
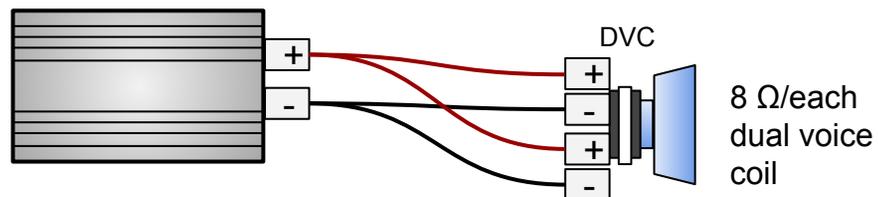
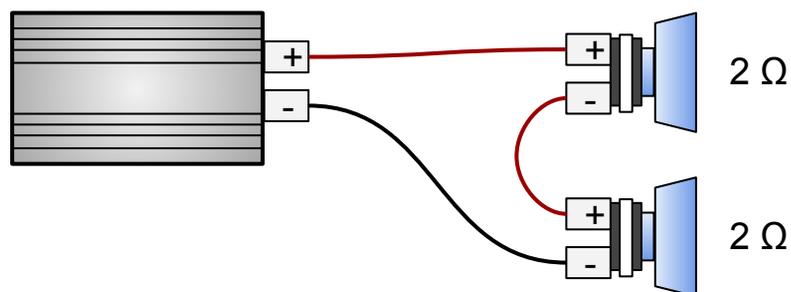
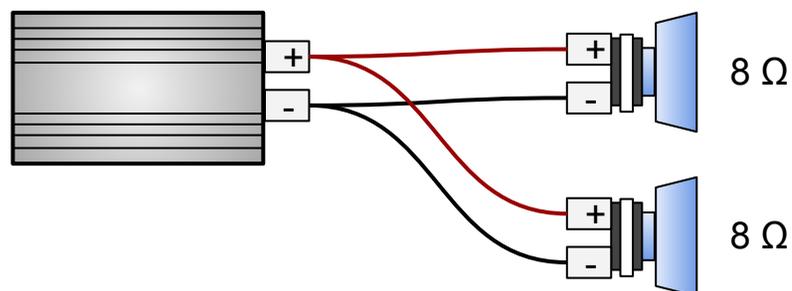


How To Bridge An Amplifier - Speaker Load Diagram And Connection Chart





www.soundcertified.com

For 4 ohm bridgeable amps:

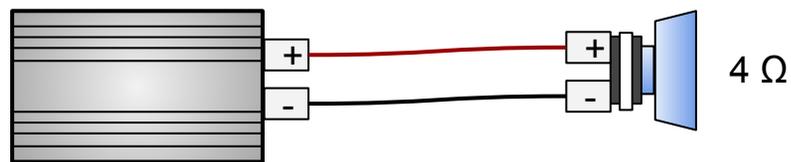(Amp with speaker connected to bridge terminals)



For 2 ohm bridgeable amps:

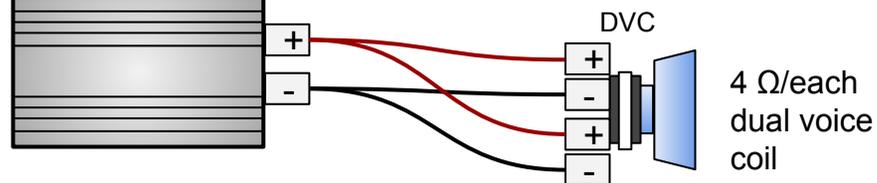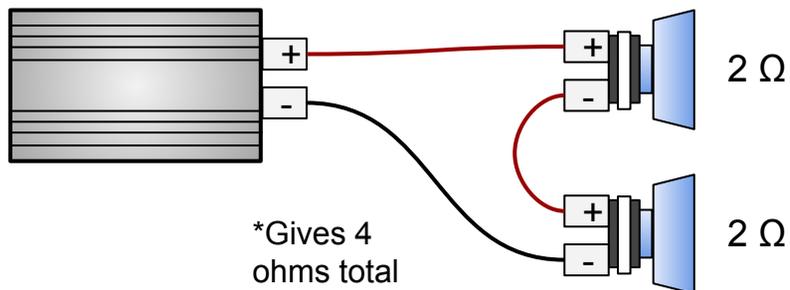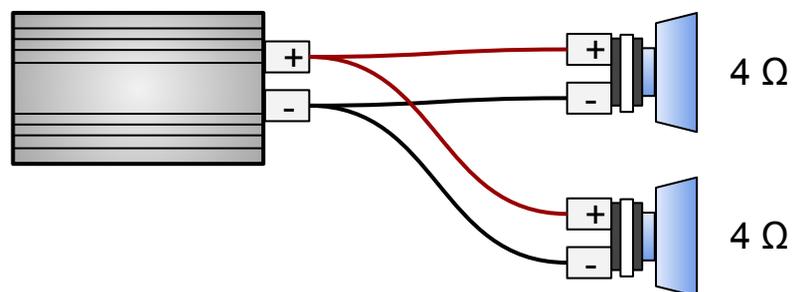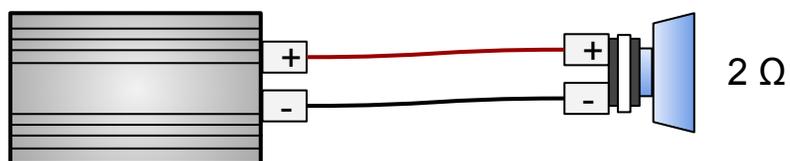

Notes:

1. Additional speakers can be used - just be sure to calculate the total load the amplifier will be connected to.
2. For 1 ohm stable bridged amps, use the same as the 2 ohm example but use 2 ohm speakers or greater